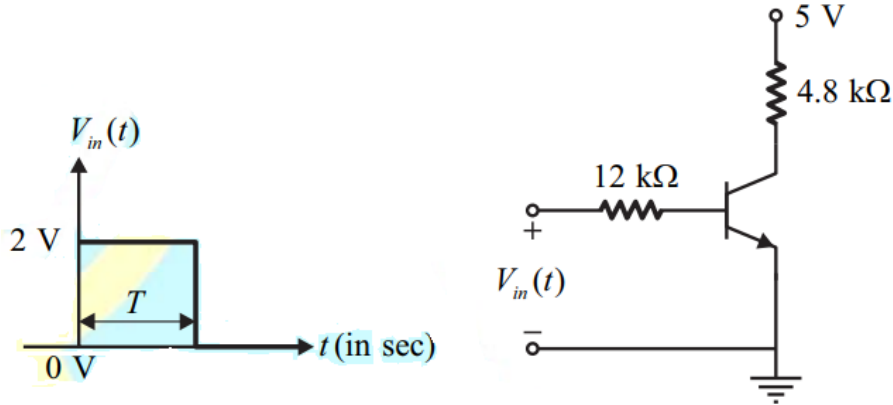


Tutorial III

Indian Institute of Technology Roorkee
Department of Electronics and Communication Engineering
EC-101: Fundamentals of Electronics, Autumn 2024


- Question:** In the figure shown, the n-p-n transistor acts as a switch




For the input V_{in} as shown in the figure, the transistor switches between the cutoff and saturation regions of operation, when T is large. Assume collector-to-emitter voltage at saturation $V_{CE(sat)} = 0.2$ V and base-to-emitter voltage $V_{BE} = 0.7$ V. What is the minimum value of the common-base current gain (α) of the transistor for the switching should be?

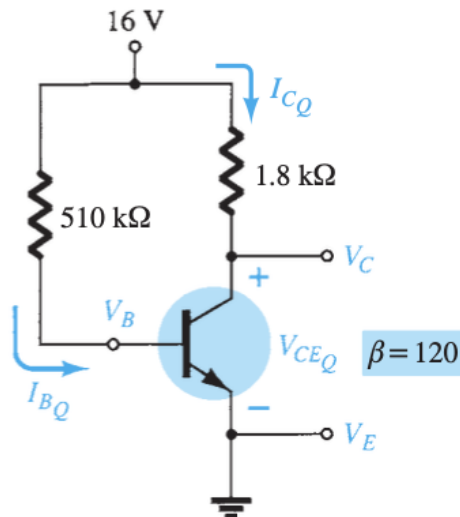- Question:** For the fixed-bias configuration, determine:

- I_{BQ}
- I_{CQ}
- V_{CEQ}
- V_C
- V_B
- V_E



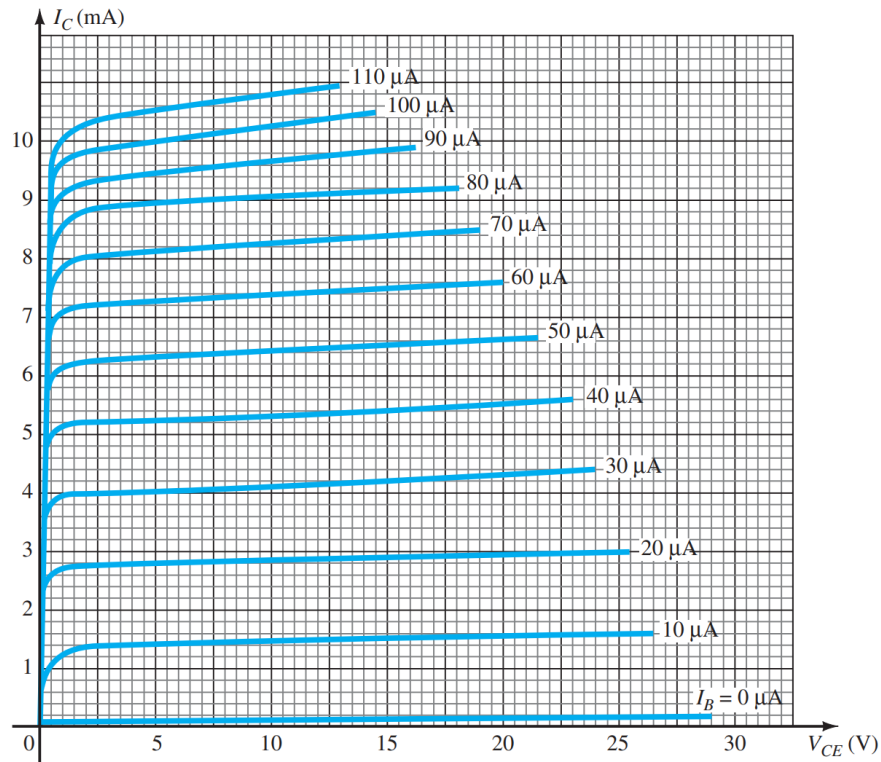
3. **Question:** Given the BJT transistor characteristics of Fig:



- Draw a load line on the characteristics determined by $E = 21$ V and $R_C = 3$ k Ω for a fixed-bias configuration.
- Choose an operating point midway between cutoff and saturation. Determine the value of R_B to establish the resulting operating point.
- What are the resulting values of I_{CQ} and V_{CEQ} ?
- What is the value of β at the operating point?
- What is the value of α defined by the operating point?
- What is the saturation current ($I_{C_{sat}}$) for the design?
- What is the DC power dissipated by the device at the operating point?
- What is the power supplied by V_{CC} ?
- Determine the power dissipated by the resistive elements by taking the difference between the results of parts (g) and (h).

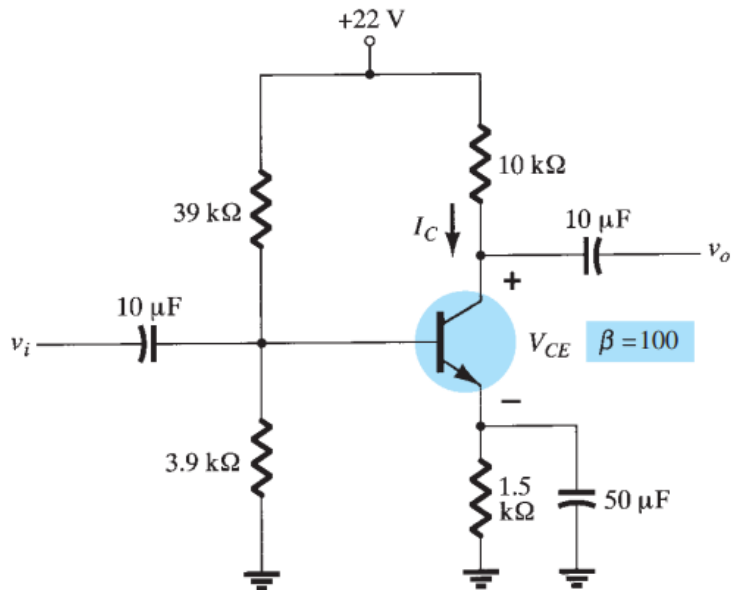4. **Question:**

- Determine the dc bias voltage V_{CE} and the current I_C for the voltage divider configuration of Fig:
- Repeat the exact analysis if β is reduced to 50, and compare solutions for I_{CQ} and V_{CEQ}



5. **Question:** Given the information provided in Figure, Determine the following:

- R_C
- R_E
- R_B
- V_{CE}
- V_B

